

*****Draft*****

12/21/18


*****Draft*****

The FPGA is used to create hardware logic using Hardware Definition Language Verilog or VHDL. The images below were found at the following site

<http://www.ee.surrey.ac.uk/Projects/CAL/digital-logic/gatesfunc/#andgate>.

The basic gates are AND, OR, NOT, NAND, NOR, EXOR, and EXNOR. These gates can be used to create FLIP FLOPS, and COUNTERS when connected together. As an example, the two NOR gates can create a SET RESET FLIP FLOP <https://www.elprocus.com/digital-electronics-flip-flop-circuit-types-and-applications/>


AND gate

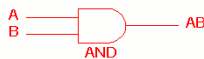

2 Input AND gate		
A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

The AND gate is an electronic circuit that gives a **high** output (1) only if **all** its inputs are high. A dot (.) is used to show the AND operation i.e. A.B. Bear in mind that this dot is sometimes omitted i.e. AB

OR gate

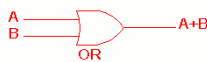


2 Input OR gate		
A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

The OR gate is an electronic circuit that gives a high output (1) if **one or more** of its inputs are high. A plus (+) is used to show the OR operation.

NOT, NAND, NOR

NOT gate

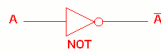


NOT gate	
A	A'
0	1
1	0

The NOT gate is an electronic circuit that produces an inverted version of the input at its output. It is also known as an *inverter*. If the input variable is A, the inverted output is known as NOT A. This is also shown as A', or A with a bar over the top, as shown at the outputs. The diagrams below show two ways that the NAND logic gate can be configured to produce a NOT gate. It can also be done using NOR logic gates in the same way.



NAND gate

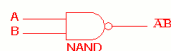

2 Input NAND gate		
A	B	A.B
0	0	1
0	1	1
1	0	1
1	1	0

This is a NOT-AND gate which is equal to an AND gate followed by a NOT gate. The outputs of all NAND gates are high if **any** of the inputs are low. The symbol is an AND gate with a small circle on the output. The small circle represents inversion.

NOR gate




2 Input NOR gate		
A	B	A+B
0	0	1
0	1	0
1	0	0
1	1	0

This is a NOT-OR gate which is equal to an OR gate followed by a NOT gate. The outputs of all NOR gates are low if **any** of the inputs are high. The symbol is an OR gate with a small circle on the output. The small circle represents inversion.

EXOR, EXNOR


EXOR gate

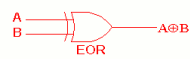

2 Input EXOR gate		
A	B	A⊕B
0	0	0
0	1	1
1	0	1
1	1	0

The 'Exclusive-OR' gate is a circuit which will give a high output if **either, but not both**, of its two inputs are high. An encircled plus sign (\oplus) is used to show the EOR operation.

EXNOR gate

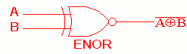

2 Input EXNOR gate		
A	B	A⊕B
0	0	1
0	1	0
1	0	0
1	1	1

The 'Exclusive-NOR' gate circuit does the opposite to the EOR gate. It will give a low output if **either, but not both**, of its two inputs are high. The symbol is an EXOR gate with a small circle on the output. The small circle represents inversion.